

Physics 2102

Lecture 12

Capacitors 2



Version: 02/09/2009






Review

- Any two charged conductors form a **capacitor**
- **Capacitance:** $C = Q/V$
- Simple Capacitors:


Parallel plates: $C = \epsilon_0 A/d$

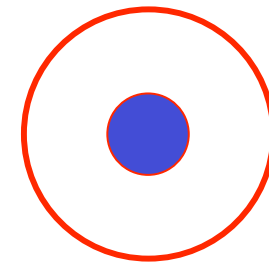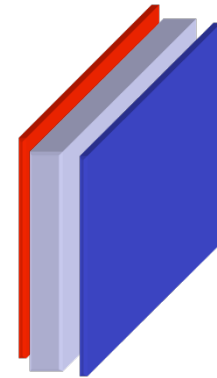Spherical: $C = 4\pi \epsilon_0 ab/(b-a)$



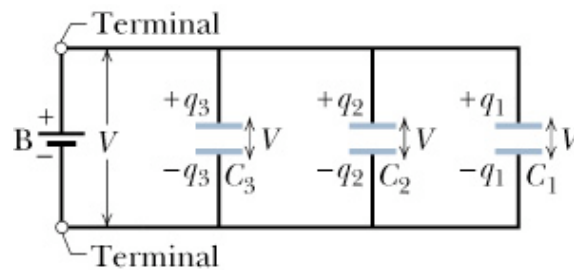


(a)

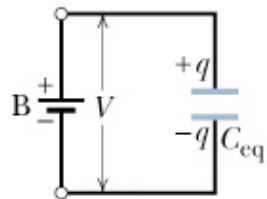


(b)

Equivalent Capacitor

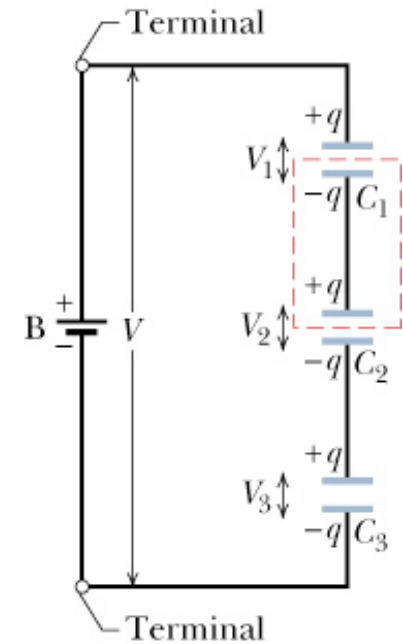Consider the combination of capacitors shown in the figure to the left and to the right (upper part). We will substitute these combinations of capacitor with a single capacitor C_{eq} that is "electrically equivalent" to the capacitor group it substitutes.




(a)

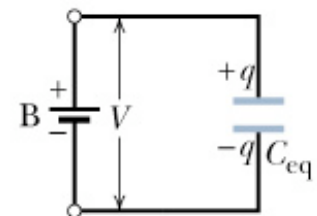

(b)

Capacitors in Parallel

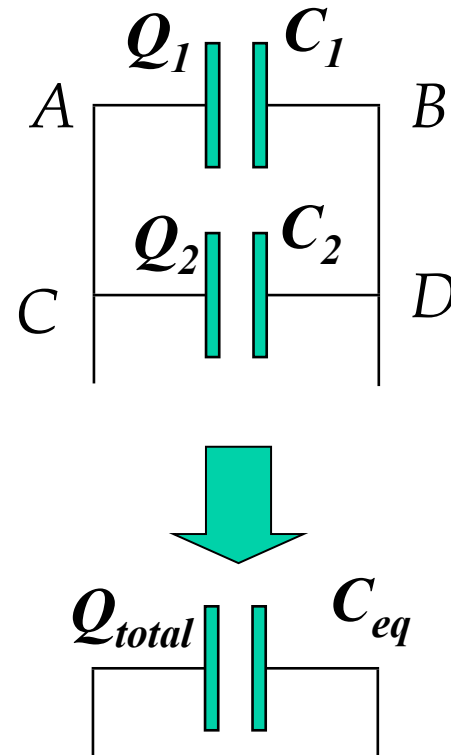- A **wire** is an equipotential surface!
- Capacitors in parallel have **same** potential difference but **not always** same charge!
- $V_{AB} = V_{CD} = V$
- $Q_{total} = Q_1 + Q_2$
- $C_{eq}V = C_1V + C_2V$
- $C_{eq} = C_1 + C_2$
- Equivalent **parallel** capacitance = sum of capacitances



Capacitors in Series


- $Q_1 = Q_2 = Q$ (WHY??)
- $V_{AC} = V_{AB} + V_{BC}$

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

SERIES:

- Q is **same** for all capacitors
- Total potential difference = sum of V

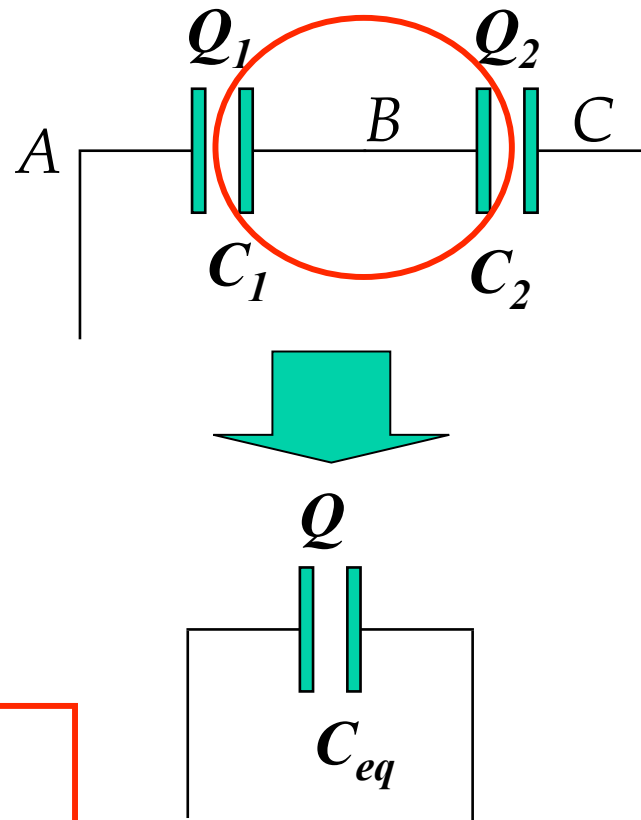


Example 1

What is the charge on each capacitor?

- $Q = CV$; $V = 120 \text{ V}$
- $Q_1 = (10 \text{ } \mu\text{F})(120\text{V}) = 1200 \text{ } \mu\text{C}$
- $Q_2 = (20 \text{ } \mu\text{F})(120\text{V}) = 2400 \text{ } \mu\text{C}$
- $Q_3 = (30 \text{ } \mu\text{F})(120\text{V}) = 3600 \text{ } \mu\text{C}$

Note that:

- Total charge ($7200 \text{ } \mu\text{C}$) is shared between the 3 capacitors in the ratio $C_1:C_2:C_3$ — i.e. 1:2:3

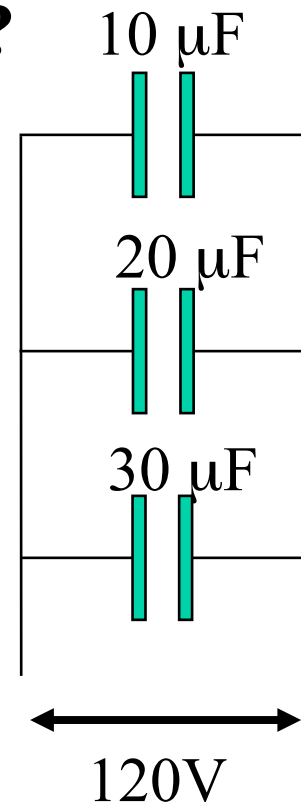


Example 2

What is the potential difference across each capacitor?

- $Q = CV$; Q is same for all capacitors
- Combined C is given by:
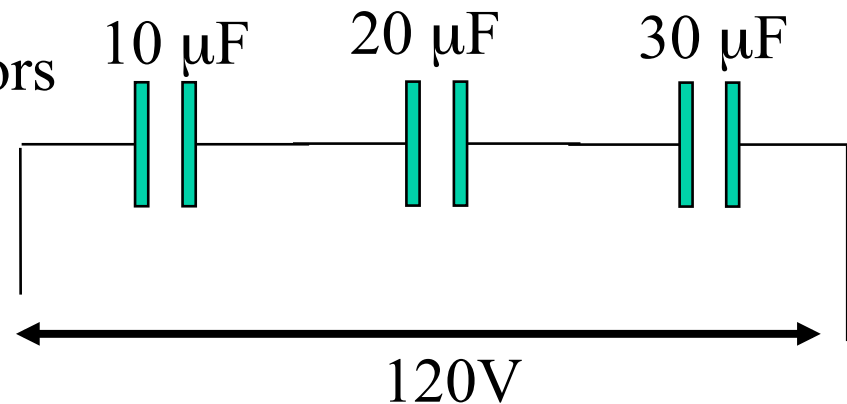
$$\frac{1}{C_{eq}} = \frac{1}{(10\mu F)} + \frac{1}{(20\mu F)} + \frac{1}{(30\mu F)}$$




- $C_{eq} = 5.46 \mu F$
- $Q = CV = (5.46 \mu F)(120V) = 655 \mu C$
- $V_1 = Q/C_1 = (655 \mu C)/(10 \mu F) = 65.5 V$
- $V_2 = Q/C_2 = (655 \mu C)/(20 \mu F) = 32.75 V$
- $V_3 = Q/C_3 = (655 \mu C)/(30 \mu F) = 21.8 V$

Note: 120V is shared in the ratio of **inverse** capacitances i.e. $1:(1/2):(1/3)$ (largest C gets smallest V)

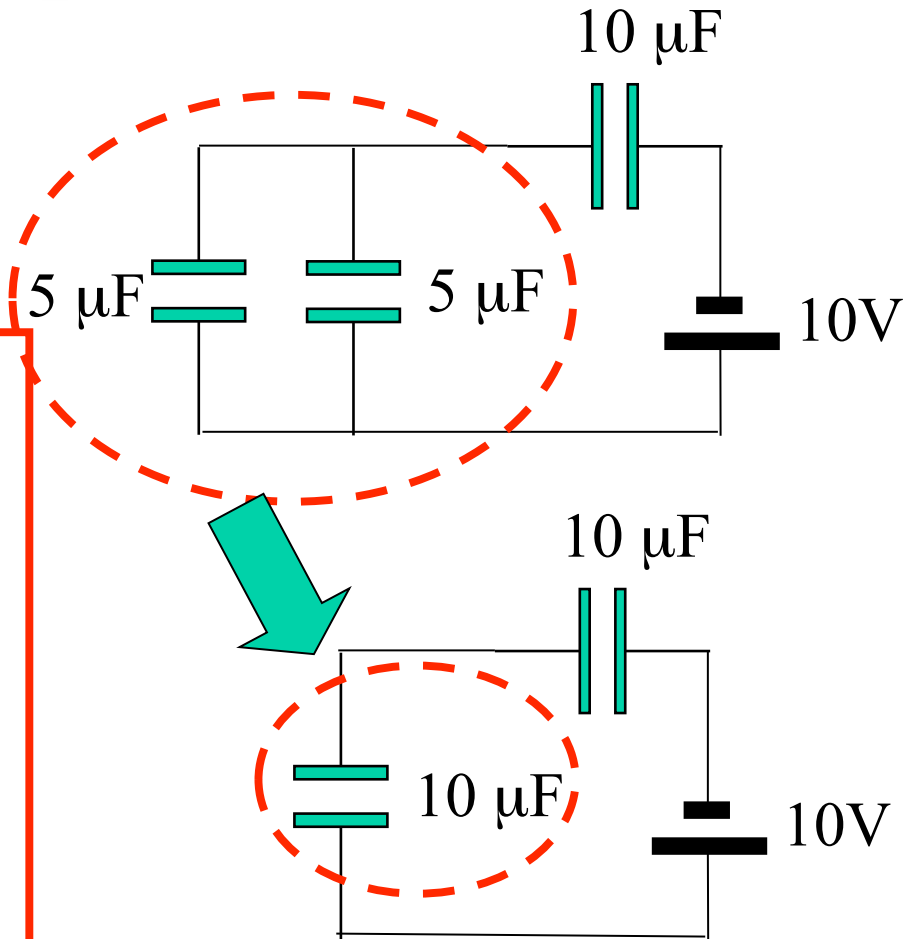Example 3


In the circuit shown, what is the charge on the $10\mu\text{F}$ capacitor?

- The two $5\mu\text{F}$ capacitors are in parallel
- Replace by $10\mu\text{F}$
- Then, we have two $10\mu\text{F}$ capacitors in series
- So, there is 5V across the $10\mu\text{F}$ capacitor of interest
- Hence, $Q = (10\mu\text{F})(5\text{V}) = 50\mu\text{C}$



Energy Stored in a Capacitor

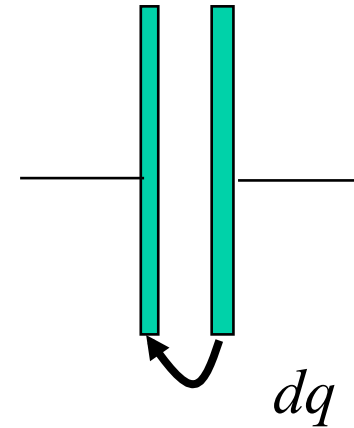- Start out with **uncharged** capacitor
- Transfer **small amount** of charge dq from one plate to the other **until** charge on each plate has magnitude Q
- How much **work** is needed?



$$U = \int_0^Q V dq = \int_0^Q \frac{q}{C} dq = \frac{Q^2}{2C} = \frac{CV^2}{2}$$

Energy Stored in Electric Field

- Energy in capacitor: $U = Q^2/(2C) = CV^2/2$
- View the energy as stored in **electric field**
- For example, parallel plate capacitor: **energy density** = energy/volume = u


$$u = \frac{Q^2}{2CAd} = \frac{Q^2}{2\left(\frac{\epsilon_0 A}{d}\right)Ad} = \frac{Q^2}{2\epsilon_0 A^2} = \frac{\epsilon_0}{2} \left(\frac{Q}{\epsilon_0 A} \right)^2 = \frac{\epsilon_0 E^2}{2}$$

volume = Ad

General expression for any region with vacuum (or air)

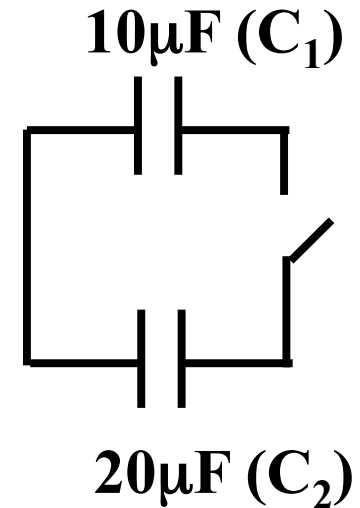Example

- $10\mu\text{F}$ capacitor is initially charged to 120V .
 $20\mu\text{F}$ capacitor is initially uncharged.
- Switch is closed, equilibrium is reached.
- How much energy is dissipated in the process?



Initial charge on $10\mu\text{F}$: $(10\mu\text{F})(120\text{V}) = 1200\mu\text{C}$

After switch is closed, let charges = Q_1 and Q_2 .

Charge is conserved: $Q_1 + Q_2 = 1200\mu\text{C}$

Also, V_{final} is same: $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \Rightarrow Q_1 = \frac{Q_2}{2} \Rightarrow$

- $Q_1 = 400\mu\text{C}$
- $Q_2 = 800\mu\text{C}$
- $V_{\text{final}} = Q_1/C_1 = 40\text{ V}$

Initial energy stored = $(1/2)C_1V_{\text{initial}}^2 = (0.5)(10\mu\text{F})(120)^2 = 72\text{mJ}$

Final energy stored = $(1/2)(C_1 + C_2)V_{\text{final}}^2 = (0.5)(30\mu\text{F})(40)^2 = 24\text{mJ}$

Energy lost (dissipated) = 48mJ

Summary

- **Capacitors in series:** same charge, not necessarily equal potential; equivalent capacitance $1/C_{eq} = 1/C_1 + 1/C_2 + \dots$
- **Capacitors in parallel:** same potential; not necessarily same charge; equivalent capacitance $C_{eq} = C_1 + C_2 + \dots$
- **Energy in a capacitor:** $U = Q^2/2C = CV^2/2$
- **Energy density:** $u = \epsilon_0 E^2/2$