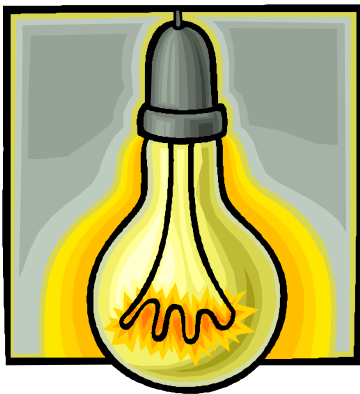



# Physics 2102

## Lecture 16

### DC Circuits 2



Version: 02/18/2009

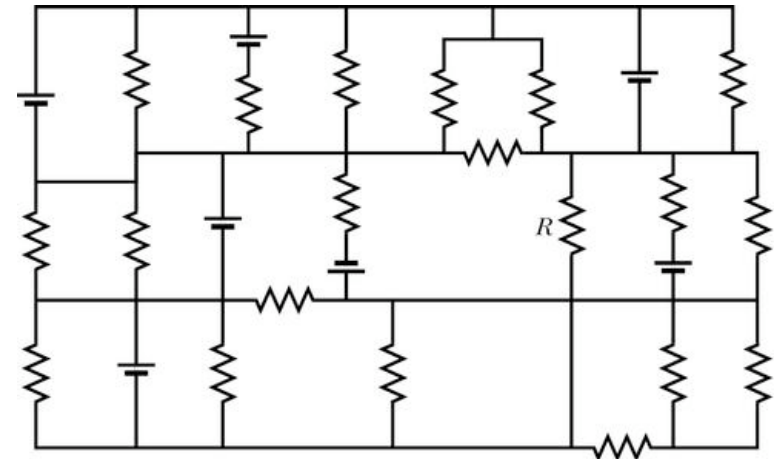


# Review

- **Electromotive force devices** (emf) maintain a potential between their terminals
- **Kirchhoff's loop rule** (KLR):


**KLR :** The algebraic sum of the changes in potential encountered in a complete traversal of any loop in a circuit is equal to zero.

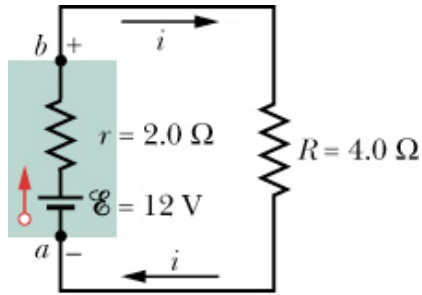- When walking through an emf, add  $+E$  if you flow with the current or  $-E$  otherwise
- When walking through a resistor, add  $-iR$ , if flowing with the current or  $+iR$  otherwise




$$V = E$$

**Ideal emf device**

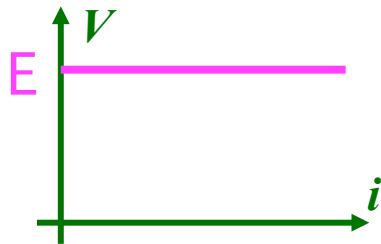

$$V = E - ir$$

**Real emf device**

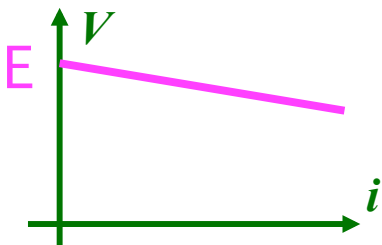

## Ideal and Real Emf Devices



An emf device is said to be **ideal** if the voltage  $V$  across its terminals  $a$  and  $b$  does **not** depend on the current  $i$  that flows through the emf device:  $V = E$ .

An emf device is said to be **real** if the voltage  $V$  across its terminals  $a$  and  $b$  **decreases** with current  $i$  according to the equation  $V = E - ir$ .

The parameter  $r$  is known as the "**internal resistance**" of the emf device.
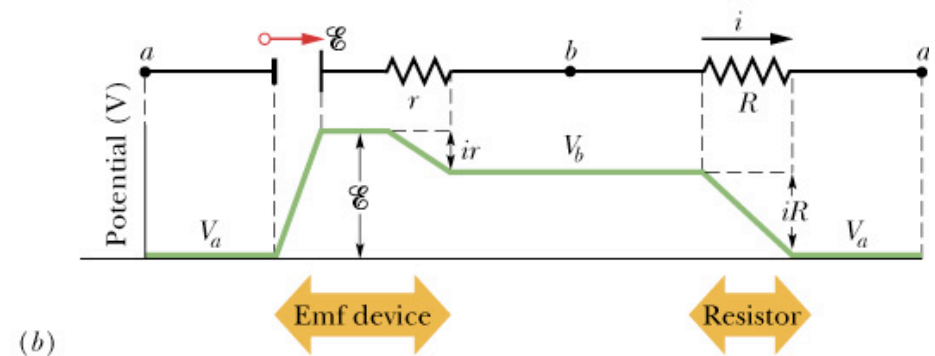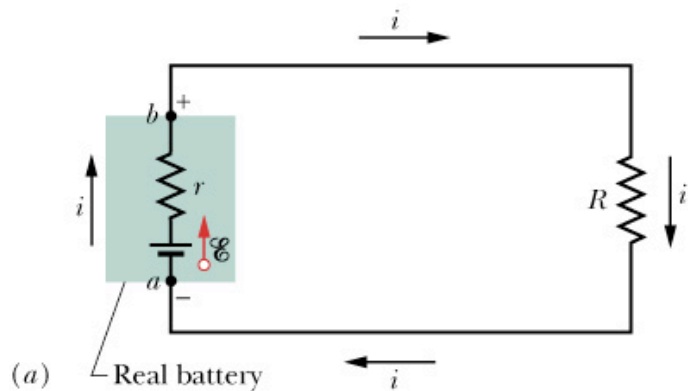
# Single Loop with Real Battery

- **Real battery** with internal resistance  $r$
- **KLR:**  $\mathcal{E} - ir - iR = 0$  yielding  $i = \mathcal{E} / (R + r)$
- For **ideal battery**  $r = 0$






# Incandescent light bulbs



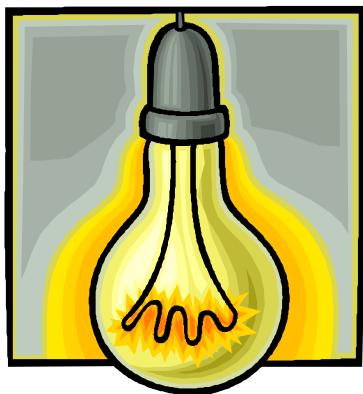- (a) Which light bulb has a smaller resistance: a 60W, or a 100W one?
- (b) Is the resistance of a light bulb different when it is on and off?
- (c) Which light bulb has a larger current through its filament: a 60W one, or a 100 W one?
- (d) Would a US light bulb be any brighter if used in Europe, using 240 V outlets?
- (e) Would a US light bulb used in Europe last more or less time?
- (f) Why do light bulbs mostly burn out when switched on?




# Resistors in Series

Two resistors are “in series” if they are connected such that the **same current** flows in both.

The “equivalent resistance” is a single imaginary resistor that can replace the resistances in series.

“Walking the loop” results in :
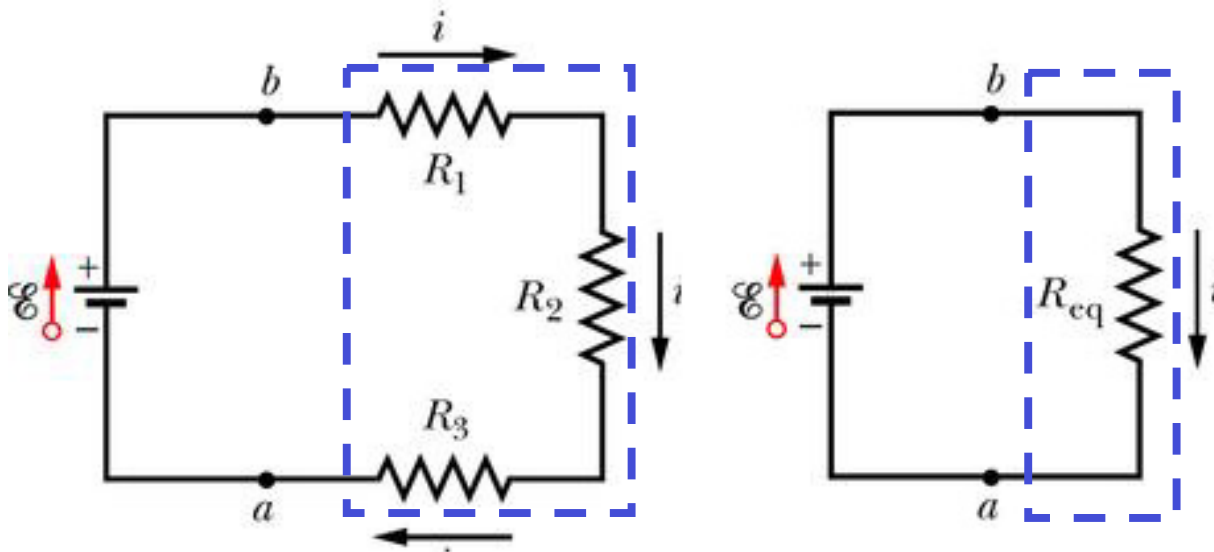
$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0 \rightarrow i = \mathcal{E} / (R_1 + R_2 + R_3)$$




In the circuit with the equivalent resistance,  
 $\mathcal{E} - iR_{eq} = 0 \rightarrow i = \mathcal{E} / R_{eq}$

Thus,

$$R_{eq} = \sum_{j=1}^n R_j$$

Behave like capacitors  
in parallel!

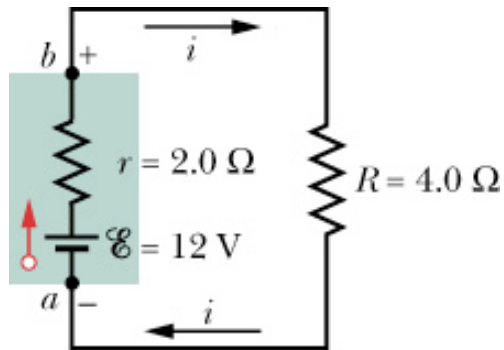

## Potential Difference Between Two Points :

Consider the circuit shown in the figure. We wish to calculate the potential difference  $V_b - V_a$  between point  $b$  and point  $a$ .

$$V_b - V_a = \text{sum of all potential changes } \Delta V \text{ along the path from point } a \text{ to point } b.$$

We choose a path in the loop that takes us from the initial point  $a$  to the final point  $b$ .

$V_f - V_i =$  sum of all potential changes  $\Delta V$  along the path.


There are two possible paths: We will try them both.

Left path:  $V_b - V_a = \mathcal{E} - ir$

Right path:  $V_b - V_a = iR$

**Note :** The values of  $V_b - V_a$  we get from the two paths are the same.


# Multiloop Circuits 1

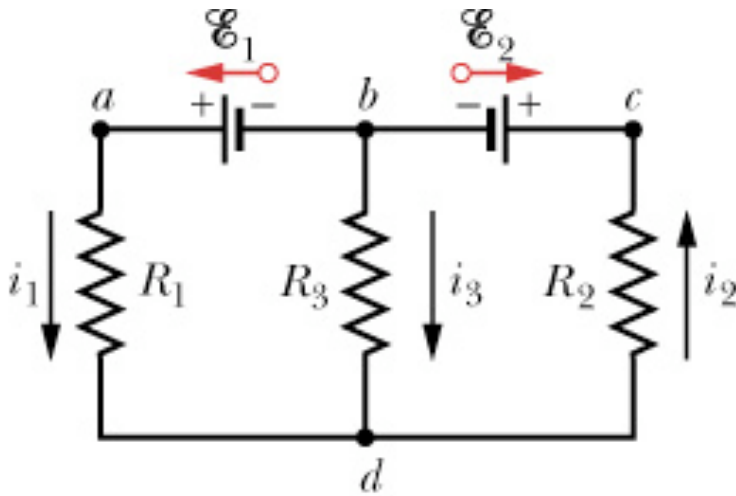

- Three branches:  $bad$ ,  $bdc$ ,  $bd$
- **Assign current directions** arbitrarily (negative currents mean opposite direction)
- Charge is conserved at point  $d$  thus  $i_1 + i_3 = i_2$  (**Kirchhoff's junction rule**: KJR)

**KJR** : The sum of the currents entering any junction is equal to the sum of the currents leaving the junction.

# Multiloop Circuits 2

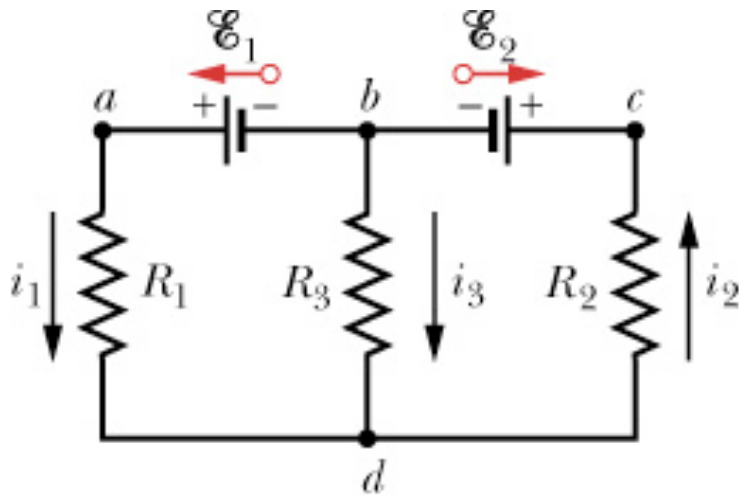

- **Need three equations** for three currents:
- 1. At *d* **KJR**:  $i_1 + i_3 = i_2$
- 2. **KLR** *bad*:  $E_1 - i_1 R_1 + i_3 R_3 = 0$
- 3. **KLR** *bdc*:  $-i_3 R_3 - i_2 R_2 - E_2 = 0$
- 4. **KLR** *badc*:  $E_1 - i_1 R_1 - i_2 R_2 - E_2 = 0$  (does not provide new information)
- **Solve** linear system of equations

# Resistors in Parallel

Two resistors are “in parallel” if they are connected such that there is the **same potential** drop through both.

The “equivalent resistance” is a single imaginary resistor that can replace the resistances in parallel.

“Walking the loops” results in :



$$\mathcal{E} - i_1 R_1 = 0, \mathcal{E} - i_2 R_2 = 0, \mathcal{E} - i_3 R_3 = 0$$

The total current delivered by the battery is  $i = i_1 + i_2 + i_3 = \mathcal{E}/R_1 + \mathcal{E}/R_2 + \mathcal{E}/R_3$ .

In the circuit with the equivalent resistor,  $i = \mathcal{E}/R_{eq}$ . Thus,


Same as capacitors  
in series.
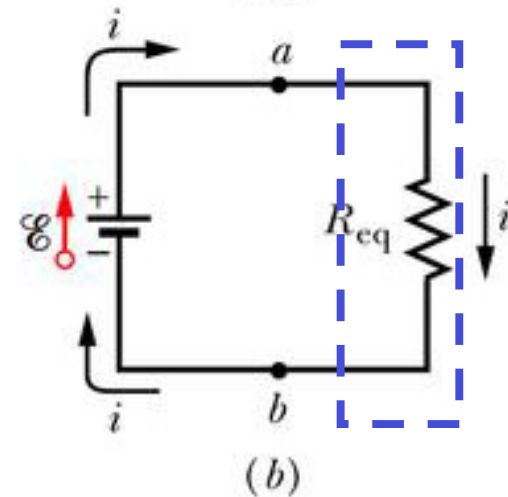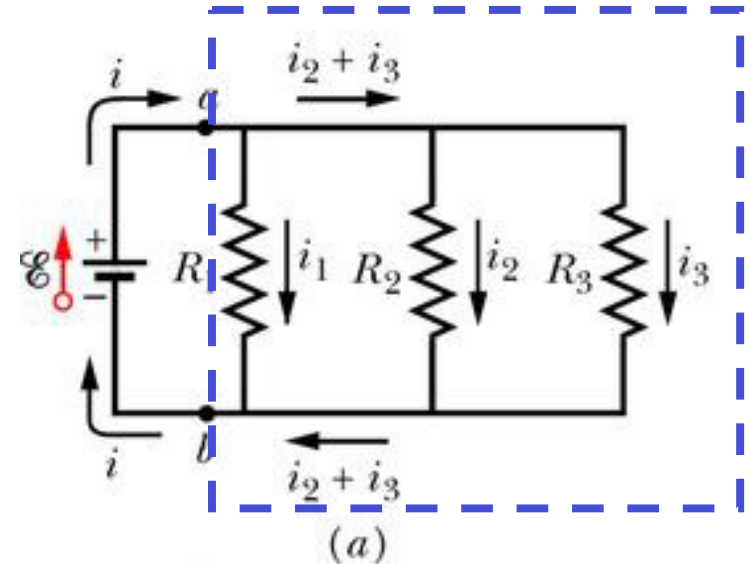
$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$




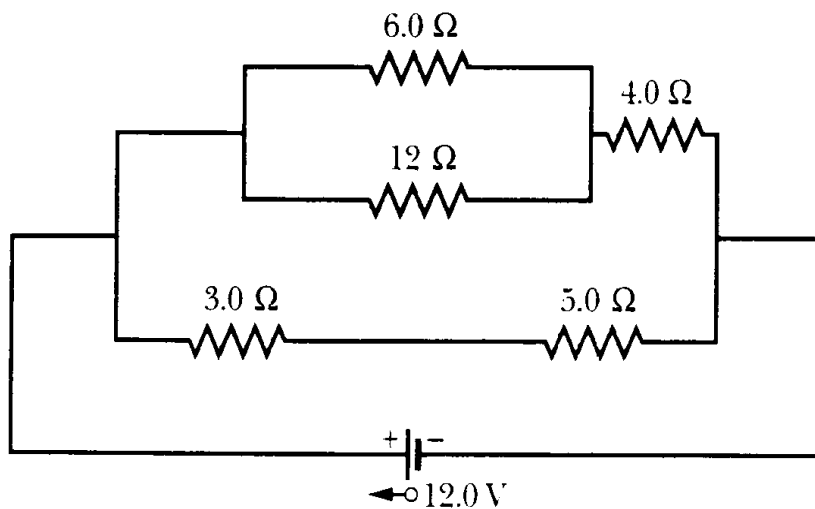
# Example

**38E.** A circuit containing five resistors connected to a battery with a 12.0 V emf is shown in Fig. 28-38. What is the potential difference across the 5.0  $\Omega$  resistor?



Bottom loop: (all else is irrelevant)

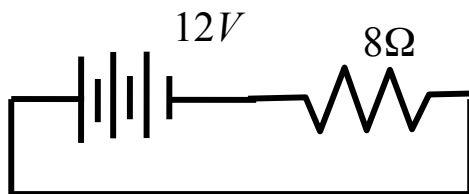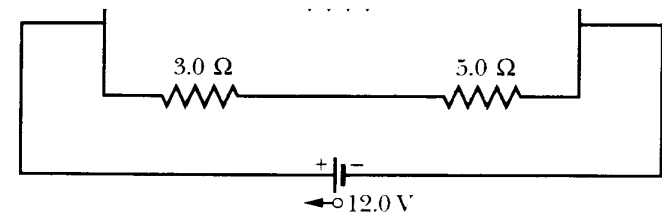

$$i = \frac{V}{R} = \frac{12V}{8\Omega} = 1.5A$$

Which resistor gets hotter?

# Resistors and Capacitors

## Resistors



Key formula:  $V=iR$


In series: same current

$$R_{eq} = \sum R_j$$



In parallel: same voltage

$$1/R_{eq} = \sum 1/R_j$$

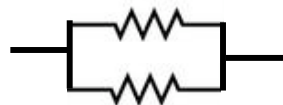

## Capacitors



$Q=CV$


same charge

$$1/C_{eq} = \sum 1/C_j$$




same voltage

$$C_{eq} = \sum C_j$$

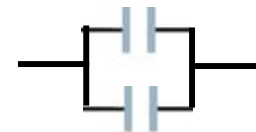

# Ammeter and Voltmeter

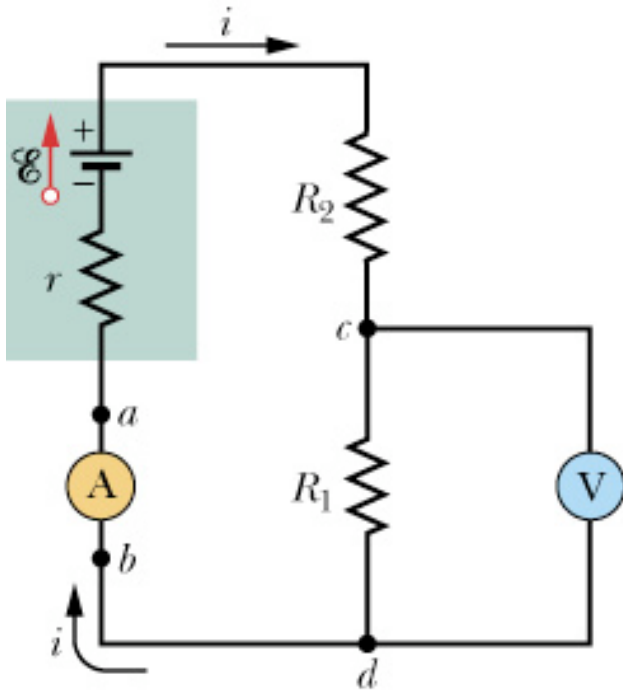

- Ammeter measures **current**
- All current flows **through** ammeter
- Resistance must be **small**
- Voltmeter measures **voltage**
- Most current **bypasses** voltmeter
- Resistance must be large

# Summary

- The potential of ideal emf devices does not depend on the current; real emf devices have **internal resistance**
- **Kirchhoff's junction rule:**

**KJR** : The sum of the currents entering any junction is equal to the sum of the currents leaving the junction.

- **Resistors in parallel** replace by equivalent resistance

$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$

- **Resistors in series** replace by equivalent resistance

$$R_{eq} = \sum_{j=1}^n R_j$$

- **Ammeter** measures current; **voltmeter** measures voltage