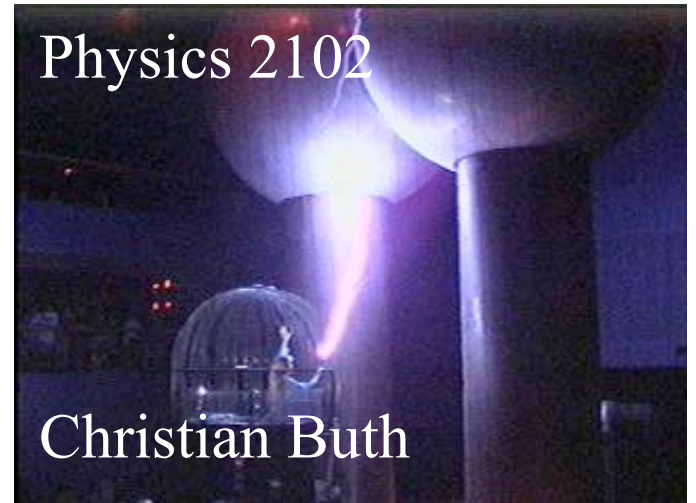


Aurora Borealis



Physics 2102

Christian Buth

Physics 2102

Lecture 20

Review Lectures 11-19

Version: 03/04/2009



"I'll be back..."




Star Quake on a

Magnetar!


Lecture 11: Capacitance 1

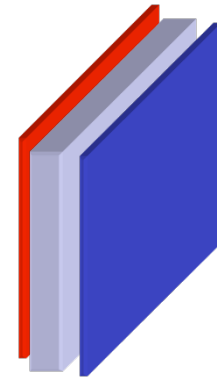- Any two charged conductors form a **capacitor**
- **Capacitance:** $C = Q/V$
- Simple Capacitors:



Parallel plates: $C = \epsilon_0 A/d$

Spherical: $C = 4\pi \epsilon_0 ab/(b-a)$

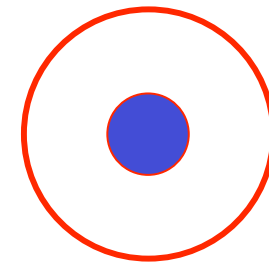

Lecture 12: Capacitance 2

- **Capacitors in series:** same charge, not necessarily equal potential; equivalent capacitance $1/C_{eq} = 1/C_1 + 1/C_2 + \dots$
- **Capacitors in parallel:** same potential; not necessarily same charge; equivalent capacitance $C_{eq} = C_1 + C_2 + \dots$
- **Energy in a capacitor:** $U = Q^2/2C = CV^2/2$
- **Energy density:** $u = \epsilon_0 E^2/2$

Lecture 13: Current and Resistance 1

- Capacitor with a dielectric: **capacitance increases** $C' = \kappa C$
- Dielectric consists of molecules which **align** in field; yields **surface charges** which reduce the field between the plates
- Battery creates **potential difference** which leads to a **current** in a closed circuit
- **Current arrow** is drawn in direction in which **positive** charge carriers would move
- **Drift speed**: v_d speed at which electrons move to establish a current

$$v_d = \frac{i}{n A e} = \frac{J}{n e}$$

$$\vec{J} = n e \vec{v}_d$$


Lecture 14: Current and Resistance 2

- A **resistor** is a conductor whose resistance does **not** change with the voltage

$$R \equiv \frac{V}{i} \qquad R = \rho \frac{L}{A}$$

- A linear $I - V$ curve is said to be **Ohmic** otherwise non-Ohmic
- **Resistivity** is associated with a **material**, **resistance** with respect to a **device** constructed with the material
- Conductivity: $\sigma = \frac{1}{\rho}$
- Resistivity depends on temperature: $\rho = \rho_0 (1 + \alpha (T - T_0))$
- Reason for resistance: conduction electrons **collide** with stationary ionic lattice

Resistance of a Rod

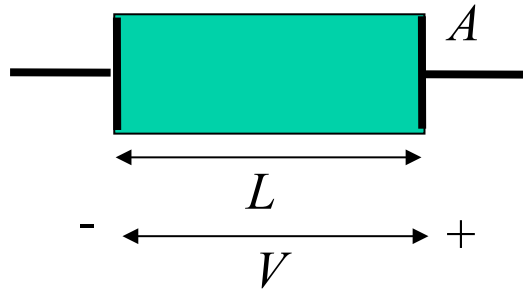

$$E = \frac{V}{L}, \quad J = \frac{i}{A}$$

$$\rho = \frac{V/L}{i/A} = R \frac{A}{L}$$

$$R = \rho \frac{L}{A}$$

Makes sense!

For a given material:

Longer \rightarrow More resistance

Thicker \rightarrow Less resistance

Lecture 15: DC Circuits 1

- **Electromotive force devices** (emf) maintain a potential between their terminals
- **Kirchhoff's loop rule** (KLR):

KLR : The algebraic sum of the changes in potential encountered in a complete traversal of any loop in a circuit is equal to zero.

- When walking through an emf, add $+E$ if you flow with the current or $-E$ otherwise
- When walking through a resistor, add $-iR$, if flowing with the current or $+iR$ otherwise

Lecture 16: DC Circuits 2

- The potential of ideal emf devices does not depend on the current; real emf devices have **internal resistance**
- **Kirchhoff's junction rule:**

KJR : The sum of the currents entering any junction is equal to the sum of the currents leaving the junction.

- **Resistors in parallel** replace by equivalent resistance

$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$

- **Resistors in series** replace by equivalent resistance

$$R_{eq} = \sum_{j=1}^n R_j$$

- **Ammeter** measures current; **voltmeter** measures voltage

Lecture 17: DC circuits, RC circuits

- Technique to **solve multiloop circuits**
 1. Simplify “compile” circuits
 2. Apply loop rule
 3. Equations to unknowns
- **RC circuits**: simple circuit with time-varying current; time constant is $\tau = RC$
- **Charging** a capacitor: $q(t) = CE(1 - e^{-t/RC})$
- **Discharging** a capacitor: $q(t) = CEe^{-t/RC}$

Step I: Simplify “Compile” Circuits

Resistors



Key formula: $V=iR$


In series: same current

$$R_{eq} = \sum R_j$$



In parallel: same voltage

$$1/R_{eq} = \sum 1/R_j$$

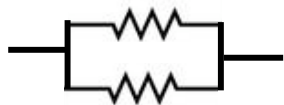

Capacitors



$$Q=CV$$



same charge

$$1/C_{eq} = \sum 1/C_j$$




same voltage

$$C_{eq} = \sum C_j$$

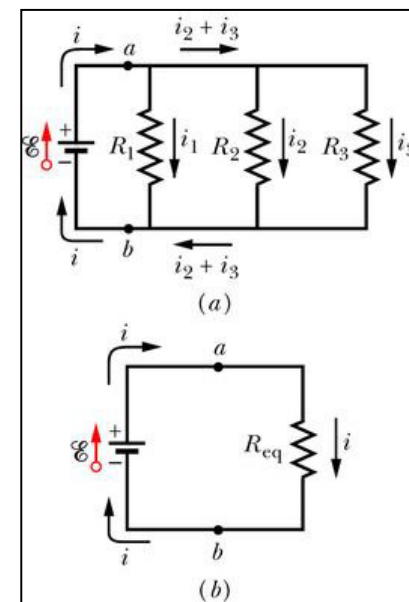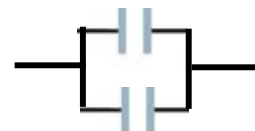

RC Circuits: Discharging a Capacitor

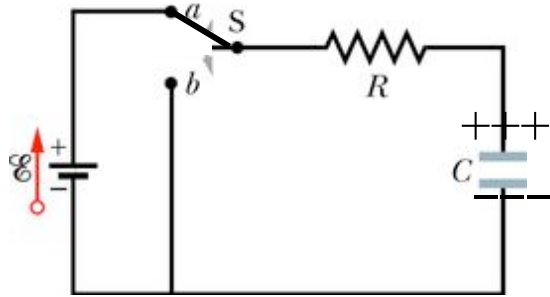

Assume the switch has been closed on *a* for a long time: the capacitor will be charged with $Q=CE$.




Then, close the switch on *b*: charges find their way across the circuit, establishing a current.

$$V_R + V_C = 0$$

$$-i(t)R - q(t)/C = 0 \Rightarrow (dq/dt)R + q(t)/C = 0$$

$$\text{Solution: } q(t) = q_0 e^{-t/RC} = CE e^{-t/RC}$$

$$i(t) = dq/dt = (q_0/RC) e^{-t/RC} = (E/R) e^{-t/RC}$$

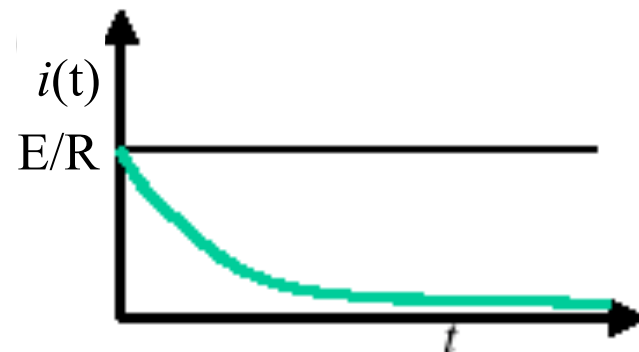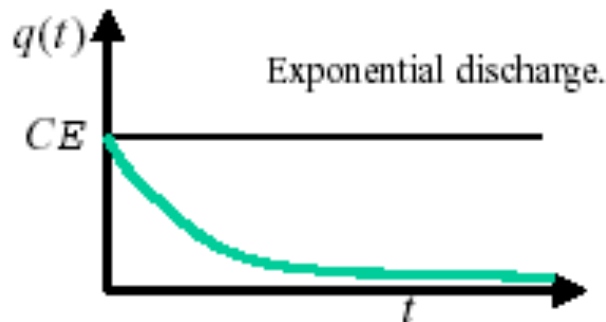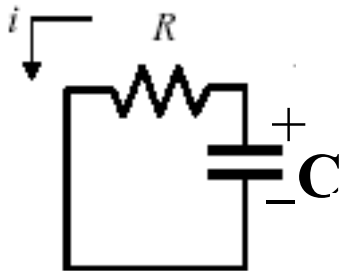

Lecture 18: Magnetic fields 1

- Magnetic fields **exert forces** on moving charges $\mathbf{F}_B = q \mathbf{v} \times \mathbf{B}$: the force is **perpendicular** to the field and the velocity
- Magnetic field lines are used to **visualize** magnetic fields
- Magnetic field \mathbf{B} has SI unit **tesla**
- **Right hand rule** for vector products (cross products)
- **Cathode ray tube** crossed electric and magnetic fields; lead to discovery of electron
- **Hall effect** reveals that charge carriers in metals are negative (electrons)

Lecture 19: Magnetic fields 2

- **Hall effect** reveals that charge carriers in metals are negative (electrons)
- Charged particle with velocity perpendicular to magnetic field on **circular path**

$$r = \frac{mv_{\perp}}{|q|B} \quad T = \frac{2\pi m}{|q|B}$$

- Generally linear and circular motion superimposed: a **helix** with radius r and **pitch** $p = Tv_{\parallel}$
- Charged particles trapped in **magnetic bottle**; natural phenomenon: **aurora borealis**
- **Cyclotrons and synchrotrons** to accelerate electron and protons



Remains to be said:

May the Force be with You!